

Power Systems Analysis

Chapter 5 Bus injection models


Outline

1. Component models
2. Network model: VI relation
3. Network model: Vs relation
4. Computation methods

Outline

1. Component models
 - Sources, impedance
 - Line
 - Transformer
2. Network model: VI relation
3. Network model: Vs relation
4. Computation methods

Overview

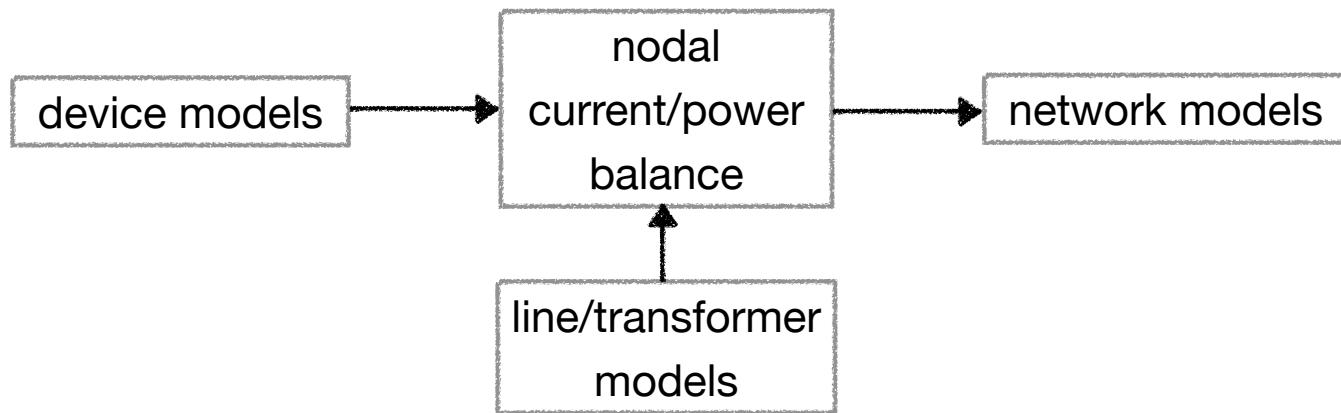

single-phase or 3-phase

Single-phase devices

1. Single-terminal device j

- Voltage source (E_j, z_j) , current source (J_j, y_j) , power source (σ_j, z_j) , impedance z_j
- Terminal variables (V_j, I_j, s_j)
- External model: relation between (V_j, I_j) or (V_j, s_j)


2. Two-terminal device (j, k)

- Line $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$, transformer $(n_{jk}, y_{jk}^s, y_{jk}^m)$
- Terminal variables (V_j, I_{jk}, S_{jk}) and (V_k, I_{kj}, S_{kj})
- External model: relation between $(V_j, V_k, I_{jk}, I_{kj})$ or $(V_j, V_k, S_{jk}, S_{kj})$

Single-phase devices

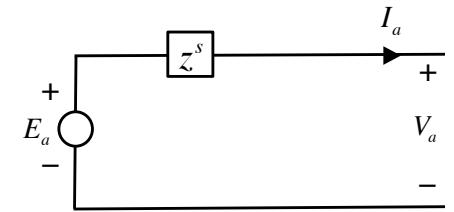1. Voltage source (E_j, z_j)


- Constant internal voltage E_j with series impedance z_j
- Models for Thevenin equivalent circuit of a balanced synchronous machine, secondary side of transformer, grid-forming inverter
- External model: $V_j = E_j - z_j I_j$
- External model: $s_j = V_j I_j^H = y_j^H V_j (E_j - V_j)^H$



Single-phase devices

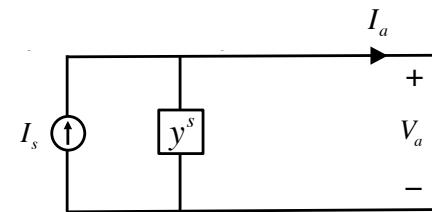2. Current source (J_j, y_j)

- Constant internal current J_j with shunt admittance y_j
- Models for Norton equivalent circuit of a synchronous generator, load (e.g. electric vehicle charger), grid-following inverter
- External model: $I_j = J_j - y_j V_j$
- External model: $s_j = V_j I_j^H = V_j (J_j - y_j V_j)^H$



Single-phase devices

3. Power source (σ_j, z_j)

- Constant internal power σ_j in series with impedance z_j
- Models for load, generator, secondary side of transformer
- External model: $\sigma_j = (V_j - z_j I_j) I_j^H$
- External model: $s_j = V_j I_j^H = \sigma_j + z_j I_j I_j^H$


Single-phase devices

4. Impedance z_j

- Constant impedance z
- Models for load
- External model: $V_j = z_j I_j$
- External model: $s_j = V_j I_j^H = \frac{|V_j|^2}{z_j^H}$

Single-phase line $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$

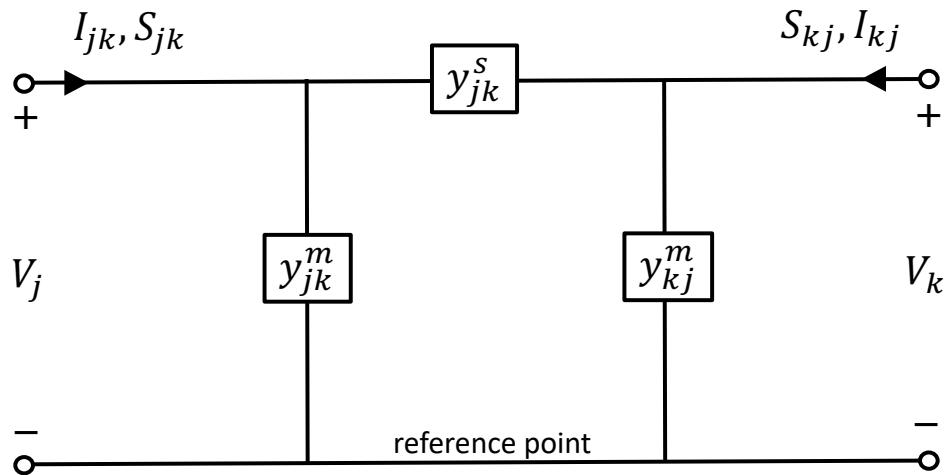VI relation: Π circuit and admittance matrix Y_{line}



$$I_{jk} = y_{jk}^s(V_j - V_k) + y_{jk}^m V_j,$$

$$I_{kj} = y_{jk}^s(V_k - V_j) + y_{kj}^m V_k$$


$$\begin{bmatrix} I_{jk} \\ I_{kj} \end{bmatrix} = \underbrace{\begin{bmatrix} y_{jk}^s + y_{jk}^m & -y_{jk}^s \\ -y_{jk}^s & y_{jk}^s + y_{kj}^m \end{bmatrix}}_{Y_{\text{line}}} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

admittance matrix Y_{line} :

- complex symmetric
- $[Y]_{jk} = -$ series admittance

Single-phase line $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$

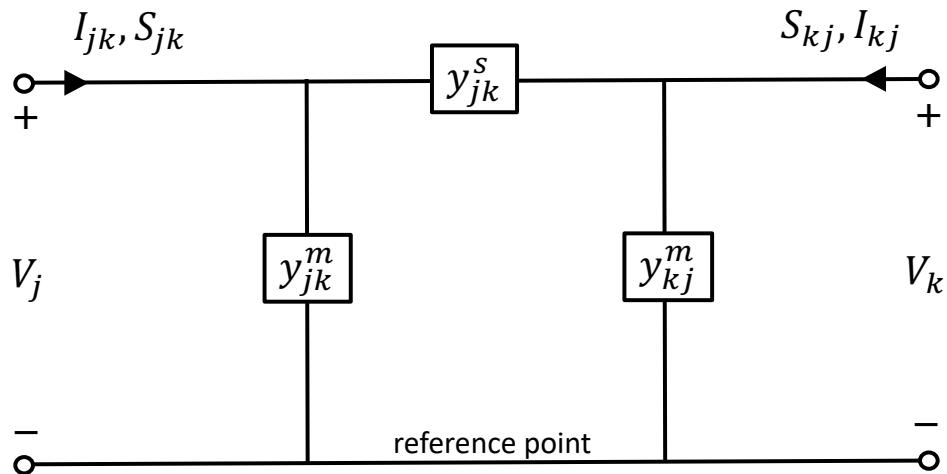VI relation: Π circuit and admittance matrix Y_{line}



$$I_{jk} = y_{jk}^s(V_j - V_k) + y_{jk}^m V_j,$$

$$I_{kj} = y_{jk}^s(V_k - V_j) + y_{kj}^m V_k$$


Their sum is total line current loss

$$I_{jk} + I_{kj} = y_{jk}^m V_j + y_{kj}^m V_k \neq 0$$

If $y_{jk}^m = y_{kj}^m = 0$, then $I_{jk} = -I_{kj}$

Single-phase line $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$

V_S relation

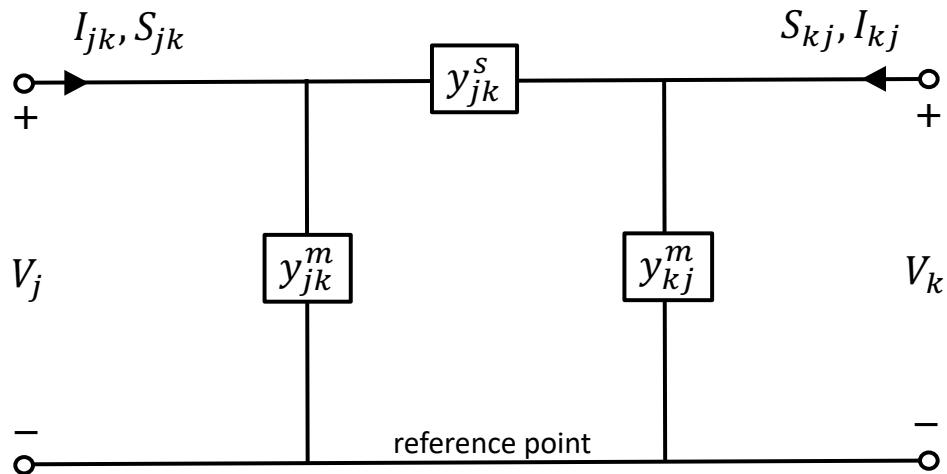


$$S_{jk} := V_j I_{jk}^H = \left(y_{jk}^s \right)^H \left(|V_j|^2 - V_j V_k^H \right) + \left(y_{jk}^m \right)^H |V_j|^2$$

$$S_{kj} := V_k I_{kj}^H = \left(y_{jk}^s \right)^H \left(|V_k|^2 - V_k V_j^H \right) + \left(y_{kj}^m \right)^H |V_k|^2$$

quadratic equations

Single-phase line $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$


***Vs* relation**

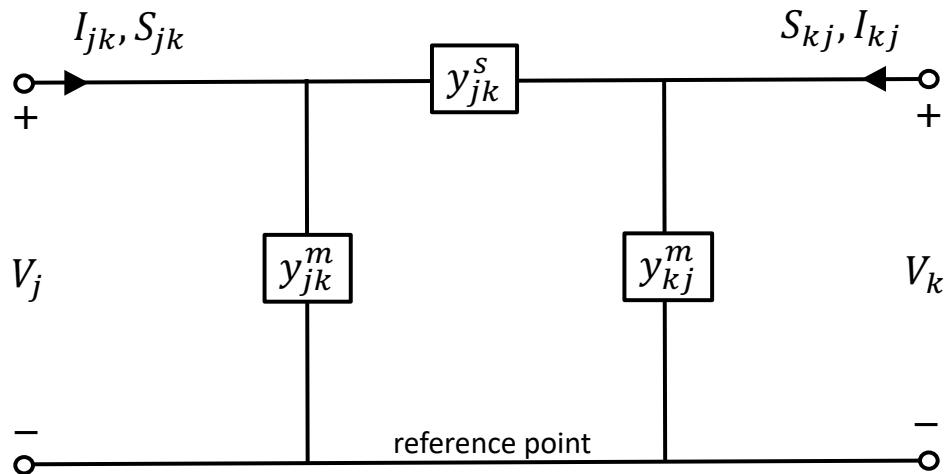

Line loss

Single-phase transformer $\left(K\left(n_{jk} \right), y_{jk}^s, y_{jk}^m \right)$

Real $K\left(n_{jk} \right) = n_{jk}$

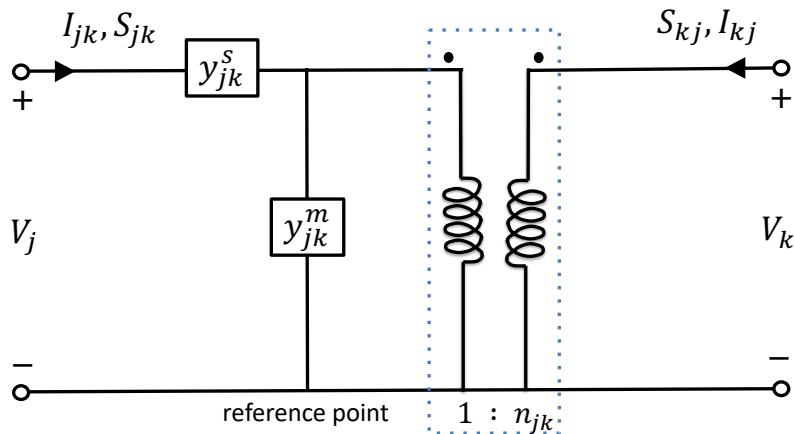

$Y_{\text{transformer}}$: complex symmetric
Hence: admittance matrix with equivalent Π circuit


$$I_{jk} = y_{jk}^s (V_j - a_{jk} V_k)$$

$$I_{kj} = y_{jk}^m a_{jk} V_k + n_{jk} (-I_{kj})$$

$$\begin{bmatrix} I_{jk} \\ I_{kj} \end{bmatrix} = \underbrace{\begin{bmatrix} y_{jk}^s & -a_{jk} y_{jk}^s \\ -a_{jk} y_{jk}^s & a_{jk}^2 (y_{jk}^s + y_{jk}^m) \end{bmatrix}}_{Y_{\text{transformer}}} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$


Single-phase transformer $\left(K\left(n_{jk} \right), y_{jk}^s, y_{jk}^m \right)$

Real $K\left(n_{jk} \right) = n_{jk}$

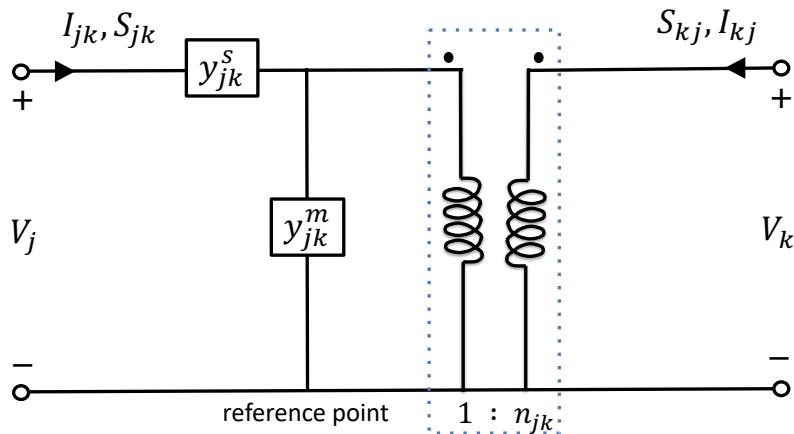

$$I_{jk} = y_{jk}^s (V_j - a_{jk} V_k)$$
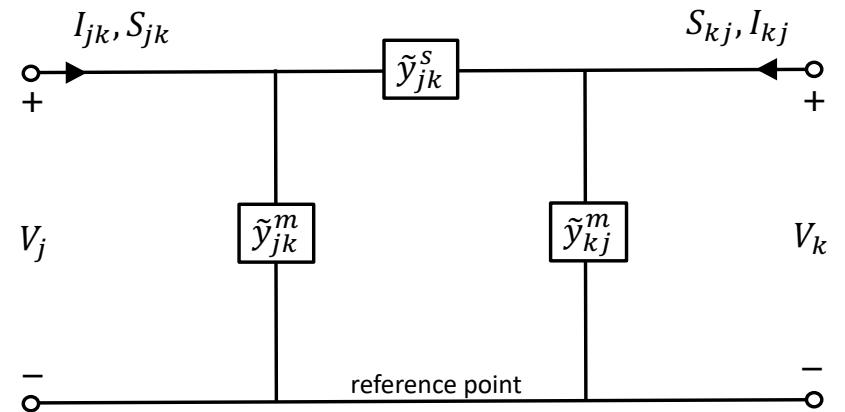
$$I_{jk} = y_{jk}^m a_{jk} V_k + n_{jk} (-I_{kj})$$



$$\tilde{y}_{jk}^s := a_{jk} y_{jk}^s$$


$$\tilde{y}_{jk}^m := (1 - a_{jk}) y_{jk}^s$$

$$\tilde{y}_{kj}^m := a_{jk} (a_{jk} - 1) y_{jk}^s + a_{jk}^2 y_{jk}^m$$

$$\tilde{y}_{jk}^m \neq \tilde{y}_{kj}^m$$

Single-phase transformer $\left(K\left(n_{jk}\right), y_{jk}^s, y_{jk}^m \right)$

Complex $K\left(n_{jk}\right)$

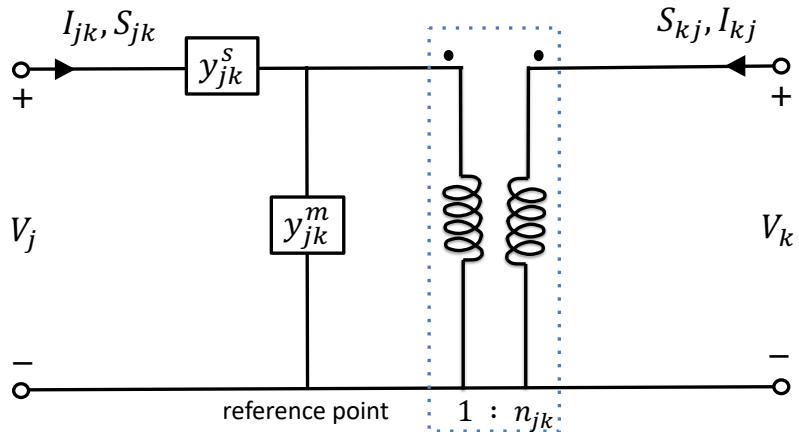


$$\begin{bmatrix} I_{jk} \\ I_{kj} \end{bmatrix} = \underbrace{\begin{bmatrix} y_{jk}^s & -y_{jk}^s/K_{jk}(n) \\ -y_{jk}^s/K_{jk}^H(n) & (y_{jk}^s + y_{jk}^m)/|K_{jk}(n)|^2 \end{bmatrix}}_{Y_{\text{transformer}}} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

- $Y_{\text{transformer}}$: not complex symmetric
- Has no equivalent Π circuit
- Use transmission matrix for analysis

Outline

1. Component models
2. Network model: VI relation
 - Examples
 - VI relation (admittance matrix Y)
 - Kron reduction
 - Invertibility of Y
3. Network model: Vs relation
4. Computation methods

Network model

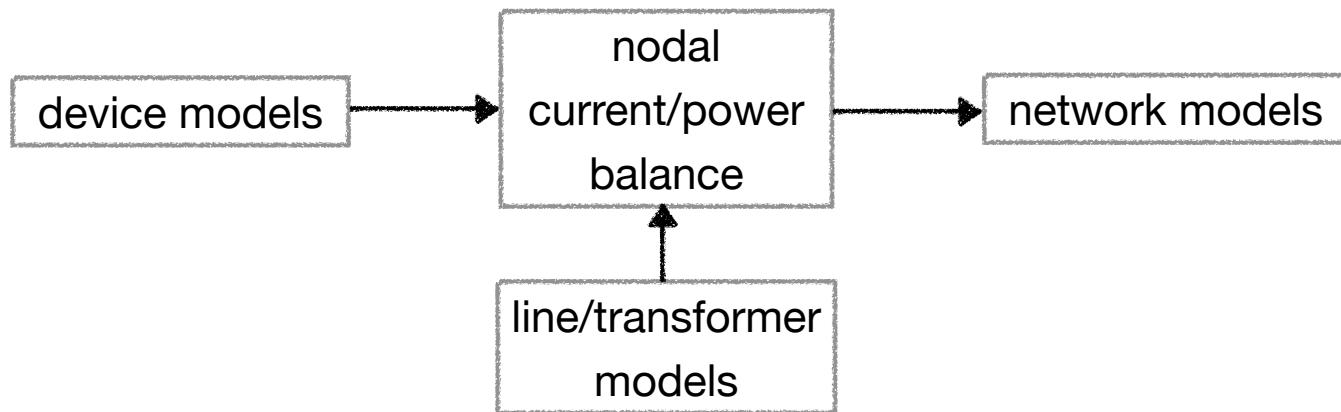

single-phase or 3-phase

Example



System

- Generator: current source (I_1, y_1)
- Transformer (n, y^l, y^m)
- Transmission line with series admittance y
- Load: current source (I_2, y_2)


Derive

- Derive network model (admittance matrix Y)

Derive Y in 2 steps

Example

Step 1: transformer + line

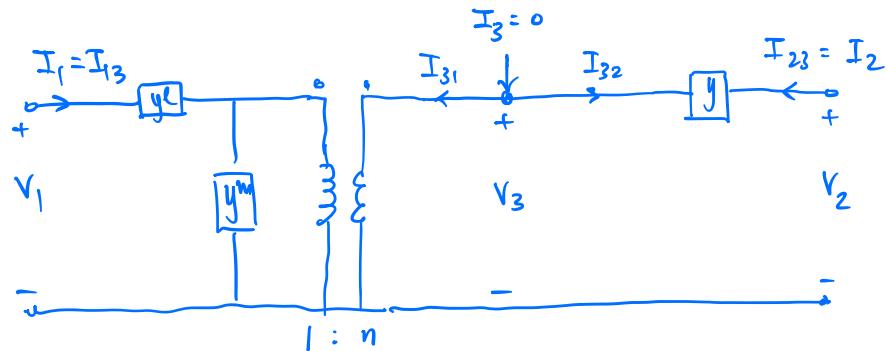

$$\begin{bmatrix} I_{13} \\ I_{31} \end{bmatrix} = \begin{bmatrix} y^l & -ay^l \\ -ay^l & a^2(y^l + y^m) \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \end{bmatrix}$$

relate branch currents with
nodal voltages

$$\begin{bmatrix} I_{32} \\ I_{23} \end{bmatrix} = \begin{bmatrix} y & -y \\ -y & y \end{bmatrix} \begin{bmatrix} V_3 \\ V_2 \end{bmatrix}$$

Nodal current balance (KCL):



$$I_1 = I_{13}$$

$$I_3 = I_{31} + I_{32} = 0$$

$$I_2 = I_{23}$$

Example

Step 1: transformer + line

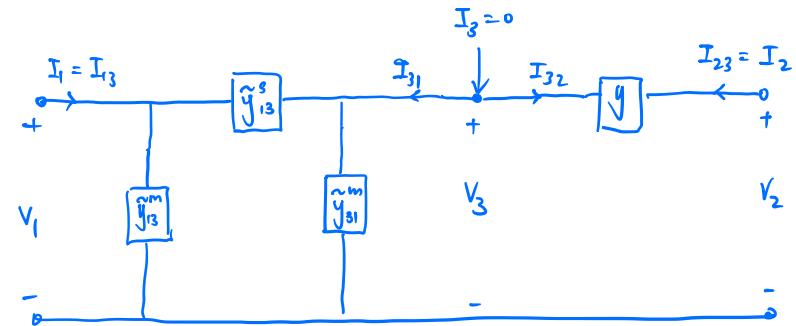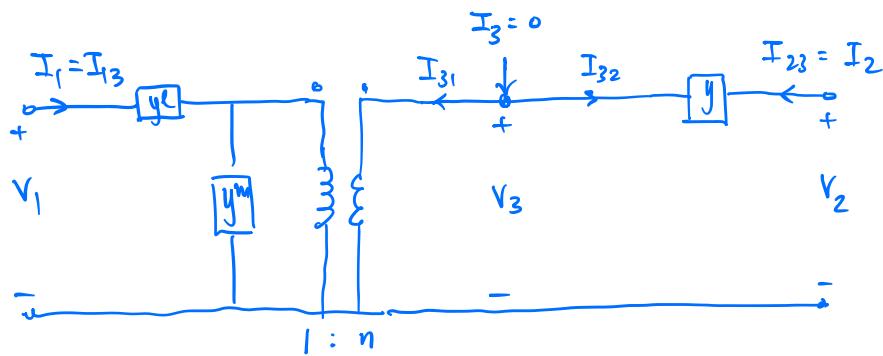


Eliminate branch currents:

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \underbrace{\begin{bmatrix} y^l & 0 & -ay^l \\ 0 & y & -y \\ -ay^l & -y & y + a^2(y^l + y^m) \end{bmatrix}}_{Y_1} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

- Y_1 : complex symmetric
- Hence: admittance matrix with Π circuit
- Unequal shunt elements


Example

Step 2: overall system

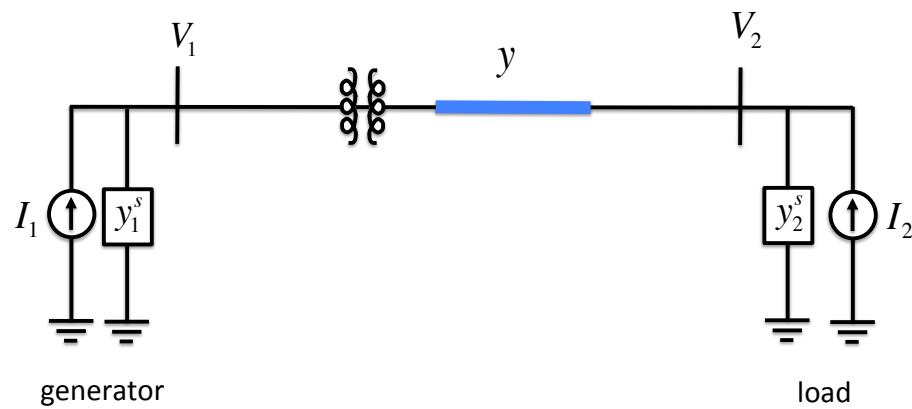

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \underbrace{\begin{bmatrix} y^l + y_1 & 0 & -ay^l \\ 0 & y + y_2 & -y \\ -ay^l & -y & y + a^2(y^l + y^m) \end{bmatrix}}_Y \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

generator/load admittances

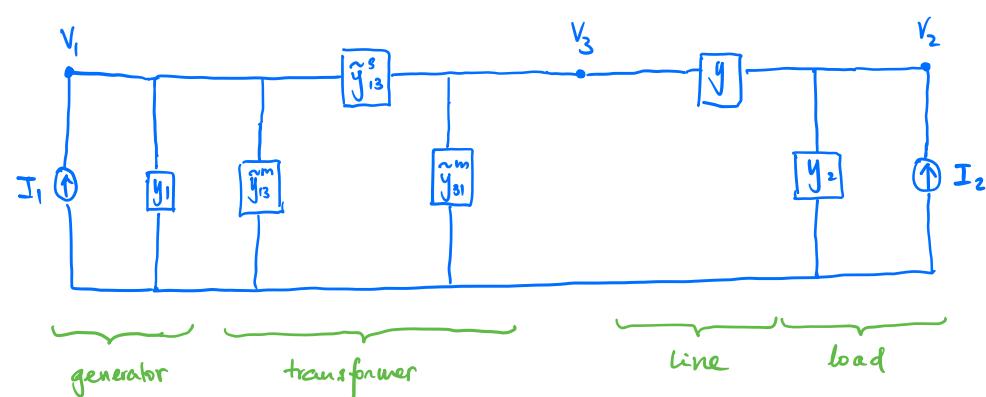


Example

Step 2: overall system



$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \underbrace{\begin{bmatrix} y^l + y_1 & 0 & -ay^l \\ 0 & y + y_2 & -y \\ -ay^l & -y & y + a^2(y^l + y^m) \end{bmatrix}}_Y \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

generator/load admittances

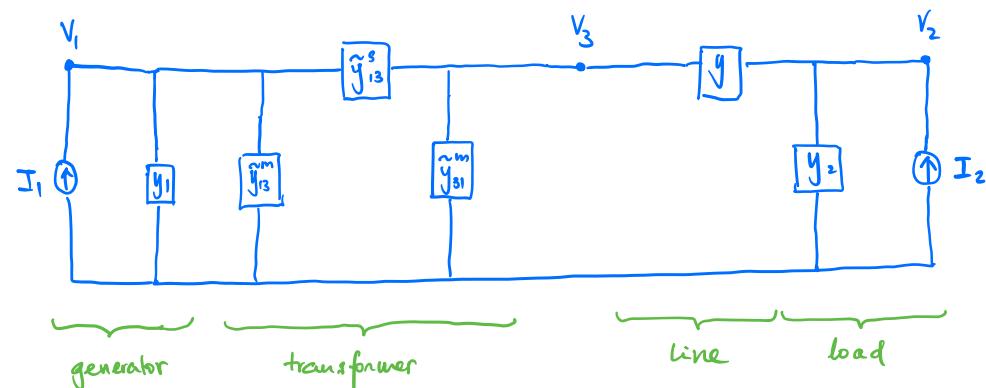

- Overall network model: **ideal** current sources connected by network
- Network: admittance matrix Y
- Y includes admittances of non-ideal current sources


Example

Step 2: overall system



$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \underbrace{\begin{bmatrix} y^l + y_1 & 0 & -ay^l \\ 0 & y + y_2 & -y \\ -ay^l & -y & y + a^2(y^l + y^m) \end{bmatrix}}_Y \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

generator/load admittances

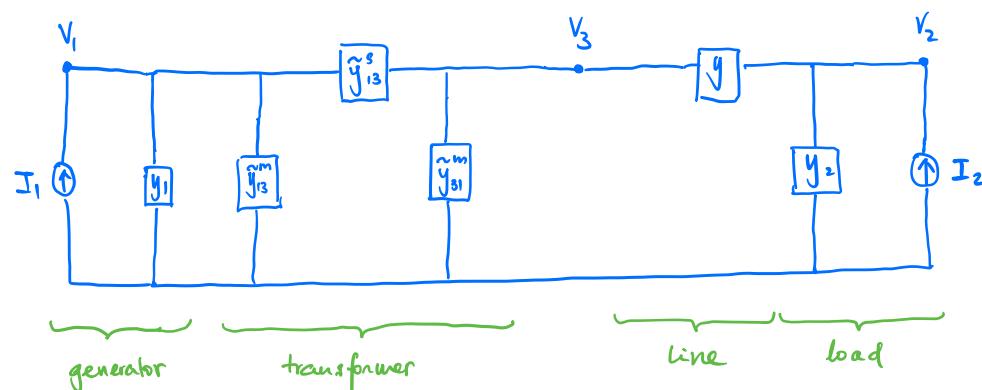

Kron reduction (see below)

- Internal bus has zero injection $I_3 = 0$
- Can eliminate (V_3, I_3)
- External behavior: relation between (I_1, I_2) and (V_1, V_2)


General network model

1. Network $G := (\bar{N}, E)$

- $\bar{N} := \{0\} \cup N := \{0\} \cup \{1, \dots, N\}$: buses/nodes/terminals
- $E \subseteq \bar{N} \times \bar{N}$: lines/branches/links/edges

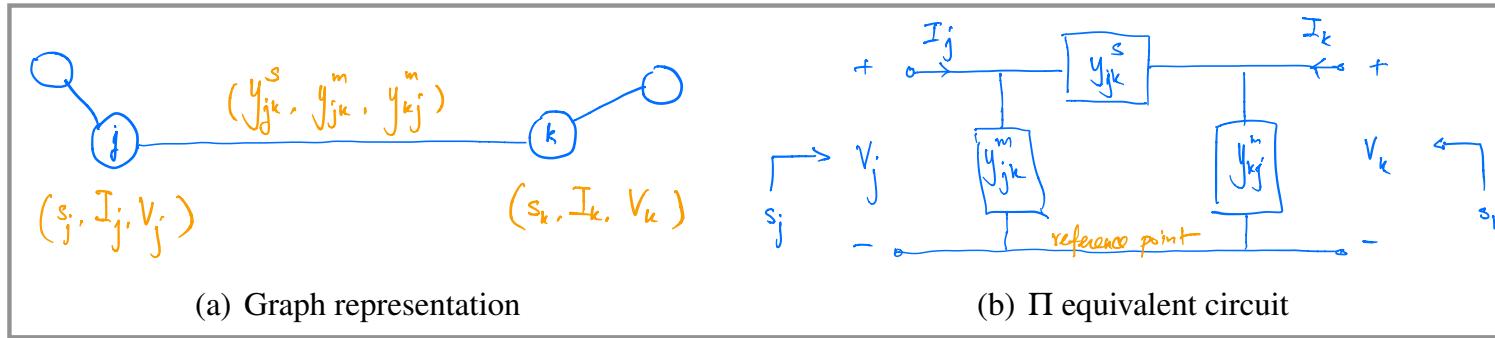
2. Each line (j, k) is parameterized by $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$

- y_{jk}^s : series admittance
- y_{jk}^m, y_{kj}^m : shunt admittances, generally different



General network model

Branch currents

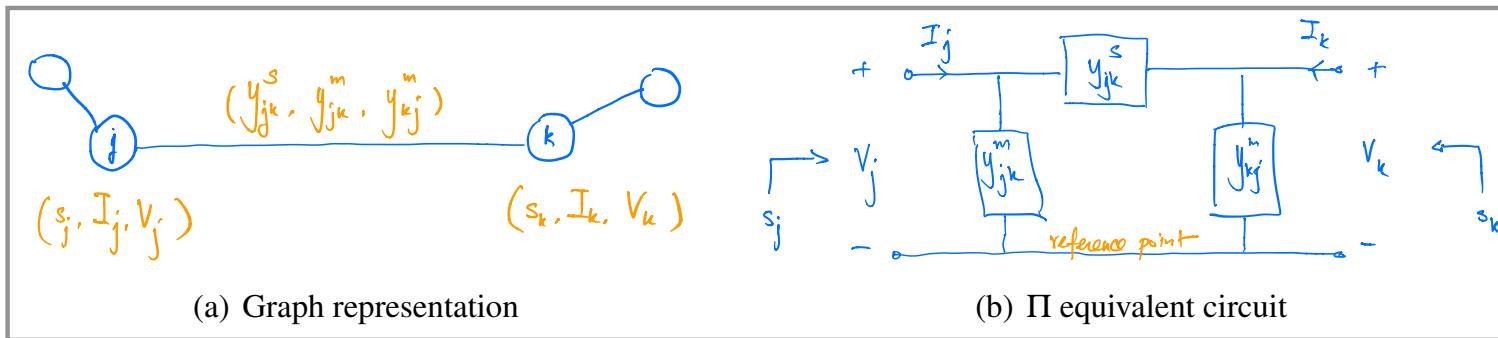


Sending-end currents

$$I_{jk} = y_{jk}^s(V_j - V_k) + y_{jk}^m V_j, \quad I_{kj} = y_{jk}^s(V_k - V_j) + y_{kj}^m V_k,$$

VI relation


Nodal current balance

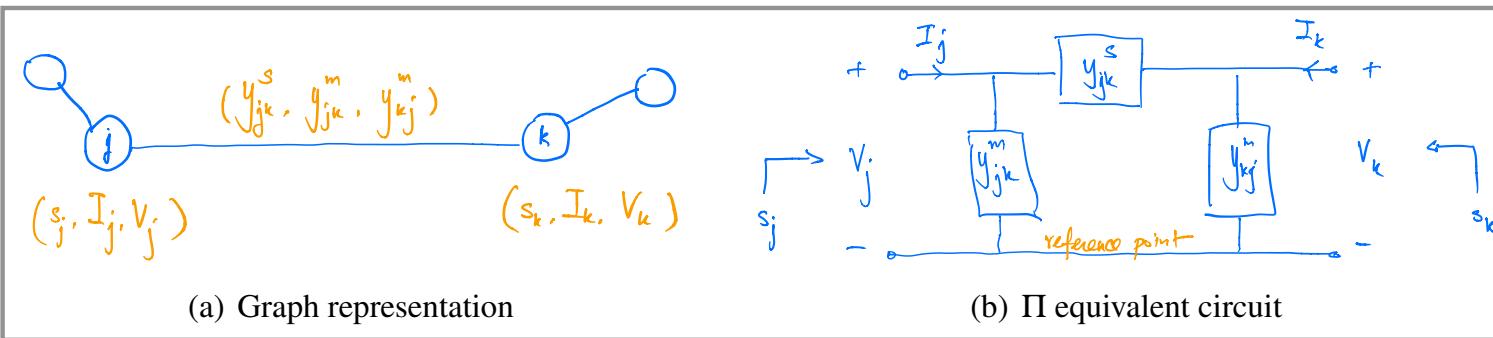

$$I_j = \sum_{k:j \sim k} I_{jk}$$

VI relation

Nodal current balance

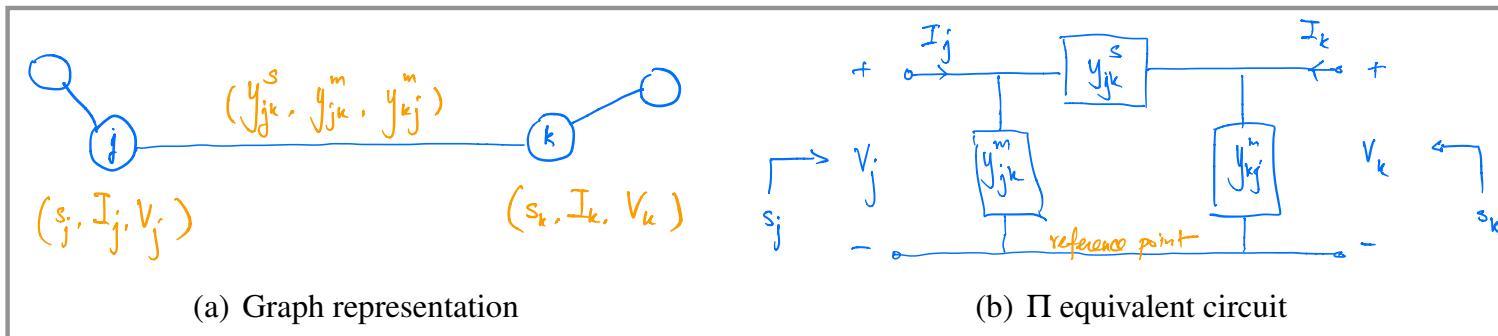

$$I_j = \sum_{k:j \sim k} I_{jk} = \left(\sum_{k:j \sim k} y_{jk}^s + y_{jj}^m \right) V_j - \sum_{k:j \sim k} y_{jk}^s V_k$$

↑
total shunt admittance: $y_{jj}^m := \sum_{k:j \sim k} y_{jk}^m$

VI relation

Admittance matrix Y

$$I_j = \sum_{k:j \sim k} I_{jk} = \left(\sum_{k:j \sim k} y_{jk}^s + y_{jj}^m \right) V_j - \sum_{k:j \sim k} y_{jk}^s V_k$$

In vector form:

$$\textcolor{blue}{I} = \textcolor{blue}{YV} \text{ where } Y_{jk} = \begin{cases} -y_{jk}^s, & j \sim k \ (j \neq k) \\ \sum_{l:j \sim l} y_{jl}^s + y_{jj}^m, & j = k \\ 0 & \text{otherwise} \end{cases}$$

VI relation

Admittance matrix Y

Y can be written down by inspection of network graph

- Off-diagonal entry: – series admittance
- Diagonal entry: \sum series admittances + total shunt admittance

In vector form:

$$I = YV \text{ where } Y_{jk} = \begin{cases} -y_{jk}^s, & j \sim k \quad (j \neq k) \\ \sum_{l:j \sim l} y_{jl}^s + y_{jj}^m, & j = k \\ 0 & \text{otherwise} \end{cases}$$

VI relation

Admittance matrix Y

A matrix Y is an admittance matrix iff it is complex symmetric


- Can be interpreted as a Π circuit

In vector form:

$$I = YV \text{ where } Y_{jk} = \begin{cases} -y_{jk}^s, & j \sim k \ (j \neq k) \\ \sum_{l:j \sim l} y_{jl}^s + y_{jj}^m, & j = k \\ 0 & \text{otherwise} \end{cases}$$

VI relation

Example

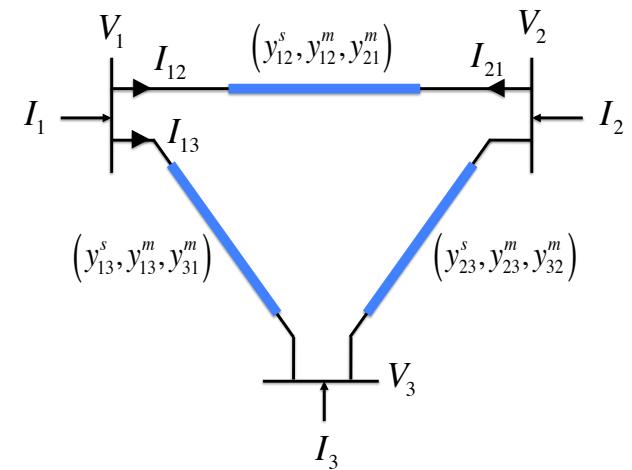

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} y_{12}^s + y_{13}^s + y_{11}^m & -y_{12}^s & -y_{13}^s \\ -y_{12}^s & y_{12}^s + y_{23}^s + y_{22}^m & -y_{23}^s \\ -y_{13}^s & -y_{23}^s & y_{13}^s + y_{23}^s + y_{33}^m \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

total shunt admittance: $y_{jj}^m := \sum_{k:j \sim k} y_{jk}^m$

Admittance matrix Y


In terms of incidence matrix C

bus-by-line incidence matrix

$$C_{jl} = \begin{cases} 1 & \text{if } l = j \rightarrow k \text{ for some bus } k \\ -1 & \text{if } l = i \rightarrow j \text{ for some bus } i \\ 0 & \text{otherwise} \end{cases}$$

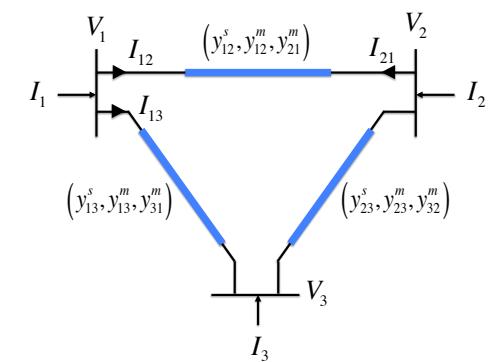example:

$$C = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$



Admittance matrix Y

In terms of incidence matrix C

bus-by-line incidence matrix

$$C_{jl} = \begin{cases} 1 & \text{if } l = j \rightarrow k \text{ for some bus } k \\ -1 & \text{if } l = i \rightarrow j \text{ for some bus } i \\ 0 & \text{otherwise} \end{cases}$$

$$Y = CY^s C^T + Y^m$$

$$\text{where } Y^s := \text{diag} \left(y_{jk}^s \right), \quad Y^m := \text{diag} \left(y_{jj}^m \right)$$

Y is a complex Laplacian matrix when $Y^m = 0$

- See later for its properties

Outline

1. Component models
2. Network model: VI relation
 - Examples
 - VI relation (admittance matrix Y)
 - Kron reduction
 - Invertibility of Y
3. Network model: Vs relation
4. Computation methods


Kron reduction

Example



$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \underbrace{\begin{bmatrix} y^l + y_1 & 0 & -ay^l \\ 0 & y + y_2 & -y \\ -ay^l & -y & y + a^2(y^l + y^m) \end{bmatrix}}_Y \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

generator/load admittances

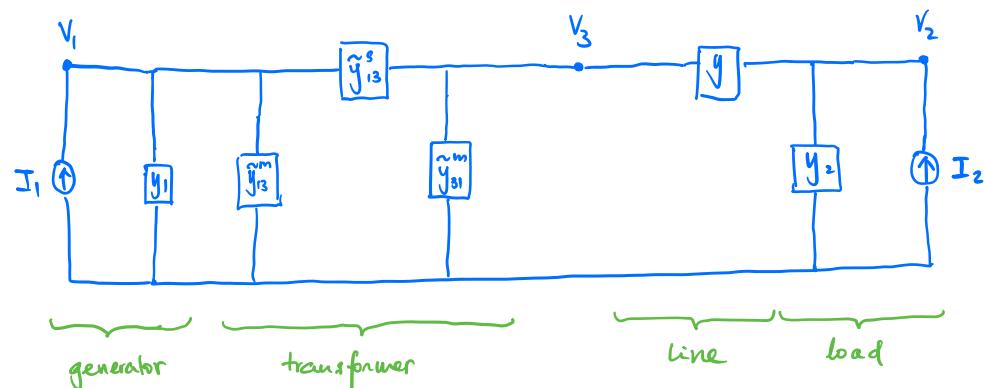

Kron reduction

- $N_{\text{red}} \subseteq \bar{N}$: buses of interest, e.g., terminal buses
- Want to relate current injections and voltages at buses in N_{red}

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}}_Y \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \begin{array}{l} \xleftarrow{N_{\text{red}}} \\ \xleftarrow{\bar{N} \setminus N_{\text{red}}} \end{array}$$

- Eliminate $V_2 = -Y_{22}^{-1}Y_{21}V_1 + Y_{22}^{-1}I_2$
- Obtain: $(Y_{11} - Y_{12}Y_{22}^{-1}Y_{21})V_1 = I_1 - Y_{12}Y_{22}^{-1}I_2$
Schur complement

Kron reduction


If internal injections $I_2 = 0$:

$$(Y_{11} - Y_{12}Y_{22}^{-1}Y_{21}) V_1 = I_1$$


Schur complement

- Describes effective connectivity and line admittances of reduced network

Example:

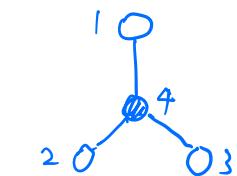

original network

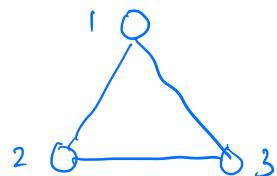

reduced network

Invertibility of Y

Zero shunt $Y^m = 0$

Admittance matrix $Y = CY^sC$ where $Y^s := \text{diag} \left(y_{jk}^s \right)$

When Y is **real**, it is called a real Laplacian matrix

- $(N + 1) \times (N + 1)$ real symmetric matrix
- Row sum = column sum = 0
- $\text{rank}(Y) = N$, $\text{null}(Y) = \text{span}(1)$
- Any principal submatrix is invertible

When Y is a complex symmetric, but not Hermitian, these properties may not hold

Invertibility of Y

Zero shunt $Y^m = 0$

Admittance matrix $Y = CY^sC$ where $Y^s := \text{diag} \left(y_{jk}^s \right)$

Theorem (Singular value decomposition)

Suppose $Y^m = 0$. Then $Y = W\Sigma W^T$ where

- Unitary W : columns are orthonormal eigenvectors of $Y\bar{Y}$ (\bar{Y} : elementwise complex conjugate of Y)
- $\Sigma := \text{diag} \left(\sigma_j \right)$: $0 = \sigma_0 \leq \sigma_1 \leq \dots \leq \sigma_N$ are nonnegative roots of eigenvalues of $Y\bar{Y}$

Pseudo-inverse $Y^\dagger := \bar{W}\Sigma^\dagger W^H$

- \bar{W} , W^H : elementwise complex conjugate and Hermitian transpose respectively of W
- $\Sigma^\dagger := \text{diag} \left(1/\sigma_j, j = 1, \dots, N \right)$ where $1/\sigma_j := 0$ if $\sigma_j = 0$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Admittance matrix $Y = CY^sC + Y^m$ where $Y^s := \text{diag} \left(y_{jk}^s \right)$, $Y^m := \text{diag} \left(y_{jj}^m \right)$

If Y^s, Y^m are real symmetric such that

- Y_{jk}^s, Y_{jj}^m are all of the same sign (e.g. for DC power flow model)

then

- Y is strictly diagonally dominant: $|Y_{jj}| = \left| \sum_{k:j \sim k} y_{jk}^s + y_{jj}^m \right| > \sum_{k:j \sim k} |y_{jk}^s|, \forall j$
- Y is therefore invertible and positive definite

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Sufficient (not necessary) condition for Y^{-1} to exist is

$$\alpha^H Y \alpha \neq 0 \text{ for all } \alpha \in C^{N+1}$$

Proof:

If Y is not invertible then it has an eigenvector α with zero eigenvalue.

$$\text{Hence } \alpha^H Y \alpha = 0$$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Sufficient (**not** necessary) condition for Y^{-1} to exist is

$$\alpha^H Y \alpha \neq 0 \text{ for all } \alpha \in C^{N+1}$$

$$\alpha^H Y \alpha = \sum_j \left(\left(\sum_{k:k \sim j} y_{jk}^s + y_{jj}^m \right) |\alpha_j|^2 - \sum_{k:k \sim j} y_{jk}^s \alpha_j^* \alpha_k \right)$$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Sufficient (not necessary) condition for Y^{-1} to exist is

$$\alpha^H Y \alpha \neq 0 \text{ for all } \alpha \in C^{N+1}$$

$$\begin{aligned} \alpha^H Y \alpha &= \sum_j \left(\left(\sum_{k:k \sim j} y_{jk}^s + y_{jj}^m \right) |\alpha_j|^2 - \sum_{k:k \sim j} y_{jk}^s \alpha_j^* \alpha_k \right) \\ &= \sum_{(j,k) \in E} y_{jk}^s \left(|\alpha_j|^2 - \alpha_j^* \alpha_k - \alpha_j \alpha_k^* + |\alpha_k|^2 \right) + \sum_{j \in \bar{N}} y_{jj}^m |\alpha_j|^2 \end{aligned}$$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Sufficient (not necessary) condition for Y^{-1} to exist is

$$\alpha^H Y \alpha \neq 0 \text{ for all } \alpha \in C^{N+1}$$

$$\begin{aligned} \alpha^H Y \alpha &= \sum_j \left(\left(\sum_{k:k \sim j} y_{jk}^s + y_{jj}^m \right) |\alpha_j|^2 - \sum_{k:k \sim j} y_{jk}^s \alpha_j^* \alpha_k \right) \\ &= \sum_{(j,k) \in E} y_{jk}^s \left(|\alpha_j|^2 - \alpha_j^* \alpha_k - \alpha_j \alpha_k^* + |\alpha_k|^2 \right) + \sum_{j \in \bar{N}} y_{jj}^m |\alpha_j|^2 \\ &= \sum_{(j,k) \in E} y_{jk}^s \left| \alpha_j - \alpha_k \right|^2 + \sum_{j \in \bar{N}} y_{jj}^m |\alpha_j|^2 \end{aligned}$$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Write $y_{jk}^s =: g_{jk}^s + i b_{jk}^s$, $y_{jj}^m =: g_{jj}^m + i b_{jj}^m$

$$\begin{aligned} \alpha^H Y \alpha &= \left(\sum_{(j,k) \in E} g_{jk}^s \left| \alpha_j - \alpha_k \right|^2 + \sum_{j \in \bar{N}} g_{jj}^m |\alpha_j|^2 \right) + \\ &\quad i \left(\sum_{(j,k) \in E} b_{jk}^s \left| \alpha_j - \alpha_k \right|^2 + \sum_{j \in \bar{N}} b_{jj}^m |\alpha_j|^2 \right) \end{aligned}$$

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Therefore Y is invertible if

1. At least one shunt admittance $y_{jj}^m \neq 0$. All nonzero g_{jj}^m (or b_{jj}^m) have same sign
2. All nonzero g_{jk}^s (or b_{jk}^s) have same sign
3. All $g_{jk}^s \neq 0$. All nonzero g_{jj}^m have the same sign as g_{jk}^s

$$\begin{aligned}\alpha^H Y \alpha &= \left(\sum_{(j,k) \in E} g_{jk}^s \left| \alpha_j - \alpha_k \right|^2 + \sum_{j \in \bar{N}} g_{jj}^m |\alpha_j|^2 \right) + i \left(\sum_{(j,k) \in E} b_{jk}^s \left| \alpha_j - \alpha_k \right|^2 + \sum_{j \in \bar{N}} b_{jj}^m |\alpha_j|^2 \right) \\ &\neq 0\end{aligned}$$

If (j, k) models a transmission line, then these sufficient conditions are satisfied

Invertibility of Y

Nonzero shunt $Y^m \neq 0$

Therefore Y is invertible if

1. At least one shunt admittance $y_{jj}^m \neq 0$. All nonzero g_{jj}^m (or b_{jj}^m) have same sign
2. All nonzero g_{jk}^s (or b_{jk}^s) have same sign
3. All $g_{jk}^s \neq 0$. All nonzero g_{jj}^m have the same sign as g_{jk}^s


Similar argument leads to sufficient conditions on invertibility of Y_{22} for Kron reduction

Outline

1. Component models
2. Network model: VI relation
3. Network model: Vs relation
 - Complex form
 - Polar form
 - Cartesian form
 - Types of buses
4. Computation methods

General network

Branch currents

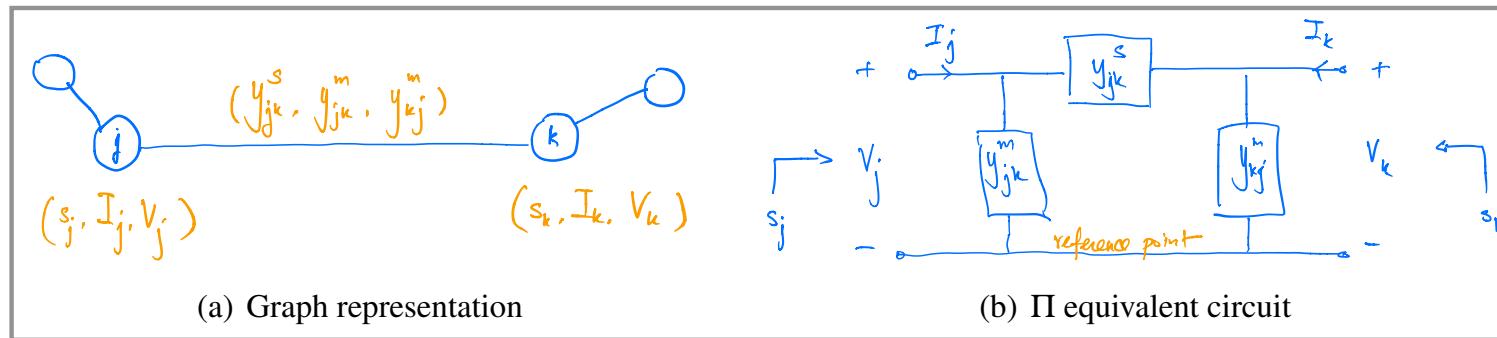

Sending-end currents

$$I_{jk} = y_{jk}^s(V_j - V_k) + y_{jk}^m V_j, \quad I_{kj} = y_{jk}^s(V_k - V_j) + y_{kj}^m V_k,$$

Power flow models

Complex form

Using $S_{jk} := V_j I_{jk}^H$:

$$S_{jk} = \left(y_{jk}^s \right)^H \left(|V_j|^2 - V_j V_k^H \right) + \left(y_{jk}^m \right)^H |V_j|^2$$

$$S_{kj} = \left(y_{jk}^s \right)^H \left(|V_k|^2 - V_k V_j^H \right) + \left(y_{kj}^m \right)^H |V_k|^2$$

Power flow models

Complex form

Bus injection model $s_j = \sum_{k:j \sim k} S_{jk}$:

$$s_j = \sum_{k:j \sim k} \left(y_{jk}^s \right)^H \left(|V_j|^2 - V_j V_k^H \right) + \left(y_{jj}^m \right)^H |V_j|^2$$

In terms of admittance matrix Y

$$s_j = \sum_{k=1}^{N+1} Y_{jk}^H V_j V_k^H$$

$N + 1$ complex equations in $2(N + 1)$ complex variables $(s_j, V_j, j \in \bar{N})$

Power flow models

Polar form

Write $s_j = p_j + iq_j$ and $V_j = |V_j| e^{i\theta_j}$ with $y_{jk}^s = g_{jk}^s + ib_{jk}^s$, $y_{jk}^m = g_{jk}^m + ib_{jk}^m$:

$$p_j = \left(\sum_{k=0}^N g_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| (g_{jk} \cos \theta_{jk} + b_{jk} \sin \theta_{jk})$$

$$q_j = - \left(\sum_{k=0}^N b_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| (g_{jk} \sin \theta_{jk} - b_{jk} \cos \theta_{jk})$$

where $g_{jk} := \begin{cases} g_{jj}^m & \text{if } j = k \\ g_{jk}^s & \text{if } j \neq k, (j, k) \in E \\ 0 & \text{if } j \neq k, (j, k) \notin E \end{cases}$ $b_{jk} := \begin{cases} b_{jj}^m & \text{if } j = k \\ b_{jk}^s & \text{if } j \neq k, (j, k) \in E \\ 0 & \text{if } j \neq k, (j, k) \notin E \end{cases}$

Power flow models

Polar form

Write $s_j := p_j + iq_j$ and $V_j =: |V_j| e^{i\phi}$ with $y_{jk}^s =: g_{jk}^s + ib_{jk}^s$, $y_{jk}^m =: g_{jk}^m + ib_{jk}^m$:

$$p_j = \left(\sum_{k=0}^N g_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| \left(g_{jk} \cos \theta_{jk} + b_{jk} \sin \theta_{jk} \right)$$

$$q_j = - \left(\sum_{k=0}^N b_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| \left(g_{jk} \sin \theta_{jk} - b_{jk} \cos \theta_{jk} \right)$$

2($N + 1$) real equations in 4($N + 1$) real variables $(p_j, q_j, |V_j|, \theta_j, j \in \overline{N})$

Power flow models

Cartesian form

Write $s_j =: p_j + iq_j$ and $V_j =: e_j + if_j$:

$$p_j = \left(\sum_k g_{jk} \right) \left(e_j^2 + f_j^2 \right) - \sum_{k \neq j} \left(g_{jk}(e_j e_k + f_j f_k) + b_{jk}(f_j e_k - e_j f_k) \right)$$

$$q_j = - \left(\sum_k b_{jk} \right) \left(e_j^2 + f_j^2 \right) - \sum_{k \neq j} \left(g_{jk}(f_j e_k - e_j f_k) - b_{jk}(e_j e_k + f_j f_k) \right)$$

2($N + 1$) real equations in 4($N + 1$) real variables $(p_j, q_j, e_j, f_j, j \in \bar{N})$

Power flow models

Types of buses

Power flow equations specify $2(N + 1)$ real equations in $4(N + 1)$ real variables

- Power flow (load flow) problem: given $2(N + 1)$ values, determine remaining vars

Types of buses

- PV buses : $(p_j, |V_j|)$ specified, determine (q_j, θ_j) , e.g. generator
- PQ buses : (p_j, q_j) specified, determine V_j , e.g. load
- Slack bus 0 : $V_0 := 1\angle0^\circ$ pu specified, determine (p_j, q_j)

Outline

1. Component models
2. Network model: VI relation
3. Network model: Vs relation
4. Computation methods
 - Gauss-Seidel algorithm
 - Newton-Raphson algorithm
 - Fast decoupled algorithm

Computation methods

Gauss-Seidel algorithm

Case 1: given V_0 and (s_1, \dots, s_N) , determine s_0 and (V_1, \dots, V_N)

Power flow equations

$$s_0 = \sum_k Y_{0k}^H V_0 V_k^H$$

$$s_j = \sum_k Y_{jk}^H V_j V_k^H, \quad j \in N$$

- First compute (V_1, \dots, V_N)
- Then compute s_0

Computation methods

Gauss-Seidel algorithm

Case 1: given V_0 and (s_1, \dots, s_N) , determine s_0 and (V_1, \dots, V_N)

Rearrange 2nd equation:

$$\frac{s_j^H}{V_j^H} = Y_{jj}V_j + \sum_{\substack{k=0 \\ k \neq j}}^N Y_{jk}V_k, \quad j \in N$$

$$V_j = \frac{1}{Y_{jj}} \left(\frac{s_j^H}{V_j^H} - \sum_{\substack{k=0 \\ k \neq j}}^N Y_{jk}V_k \right) =: f_j(V_1, \dots, V_N), \quad j \in N$$

Computation methods

Gauss-Seidel algorithm

Case 1: given V_0 and (s_1, \dots, s_N) , determine s_0 and (V_1, \dots, V_N)

2nd power flow equation:

$$V = f(V)$$

where $V := (V_j, j \in N)$, $f := (f_j, j \in N)$

Gauss algorithm is the fixed point iteration

$$V(t + 1) = f(V(t))$$

Computation methods

Gauss-Seidel algorithm

Case 1: given V_0 and (s_1, \dots, s_N) , determine s_0 and (V_1, \dots, V_N)

Gauss algorithm:

$$V_1(t+1) = f_1(V_1(t), \dots, V_N(t))$$

$$V_2(t+1) = f_2(V_1(t), \dots, V_N(t))$$

⋮

$$V_N(t+1) = f_N(V_1(t), \dots, V_{N-1}(t), V_N(t))$$

Computation methods

Gauss-Seidel algorithm

Case 1: given V_0 and (s_1, \dots, s_N) , determine s_0 and (V_1, \dots, V_N)

Gauss-Seidel algorithm:

$$V_1(t + 1) = f_1(V_1(t), \dots, V_N(t))$$

$$V_2(t + 1) = f_2(V_1(t + 1), \dots, V_N(t))$$

⋮

$$V_N(t + 1) = f_N(V_1(t + 1), \dots, V_{N-1}(t + 1), V_N(t))$$

Computation methods

Gauss-Seidel algorithm

Case 2: given (V_0, \dots, V_m) and (s_{m+1}, \dots, s_N) , determine $(s_j, j \leq m)$ and $(V_j, j > m)$

Power flow equations

$$s_j = \sum_k Y_{jk}^H V_j V_k^H, \quad j \leq m$$

$$s_j = \sum_k Y_{jk}^H V_j V_k^H, \quad j > m$$

- First compute (V_{m+1}, \dots, V_N) from 2nd set of equations using the same algorithm
- Then compute $(s_j, j \leq m)$ from 1st set of equations

Computation methods


Gauss-Seidel algorithm

If algorithm converges, the limit is a fixed point and a power flow solution


Algorithm converges linearly to unique fixed point if f is a contraction mapping

- Contraction is sufficient, but not necessary, for convergence

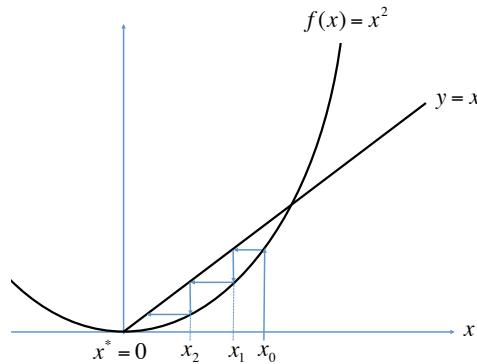In general, algorithm may or may not converge depending on initial point



(a) Convergence

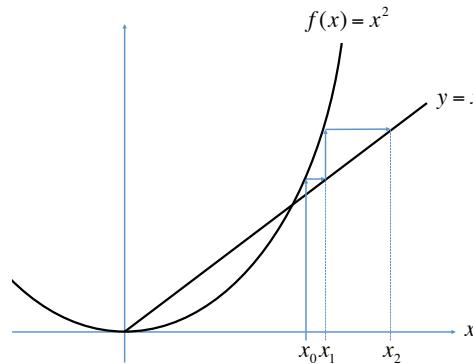

(b) Divergence

Computational methods

Newton-Raphson algorithm

To solve

$$f(x) = 0$$

where $f: \mathbb{R}^n \rightarrow \mathbb{R}^n$, e.g. $\nabla F(x) = 0$ for unconstrained optimization

Idea:

- Linear approximation

$$\hat{f}(x(t+1)) = f(x(t)) + J(x(t)) \Delta x(t)$$

- Choose $\Delta x(t)$ such that $\hat{f}(x(t+1)) = 0$, i.e., solve

$$J(x(t)) \Delta x(t) = -f(x(t))$$

- Next iterate $x(t+1) := x(t) + \Delta x(t)$

$$J(x) := \frac{\partial f}{\partial x}(x) = \begin{bmatrix} \frac{\partial f_1}{\partial x_1}(x) & \cdots & \frac{\partial f_1}{\partial x_n}(x) \\ \vdots & \ddots & \vdots \\ \frac{\partial f_n}{\partial x_1}(x) & \cdots & \frac{\partial f_n}{\partial x_n}(x) \end{bmatrix}$$

Computational methods


Newton-Raphson algorithm

To solve

$$f(x) = 0$$

where $f: \mathbb{R}^n \rightarrow \mathbb{R}^n$, e.g. $\nabla F(x) = 0$ for unconstrained optimization
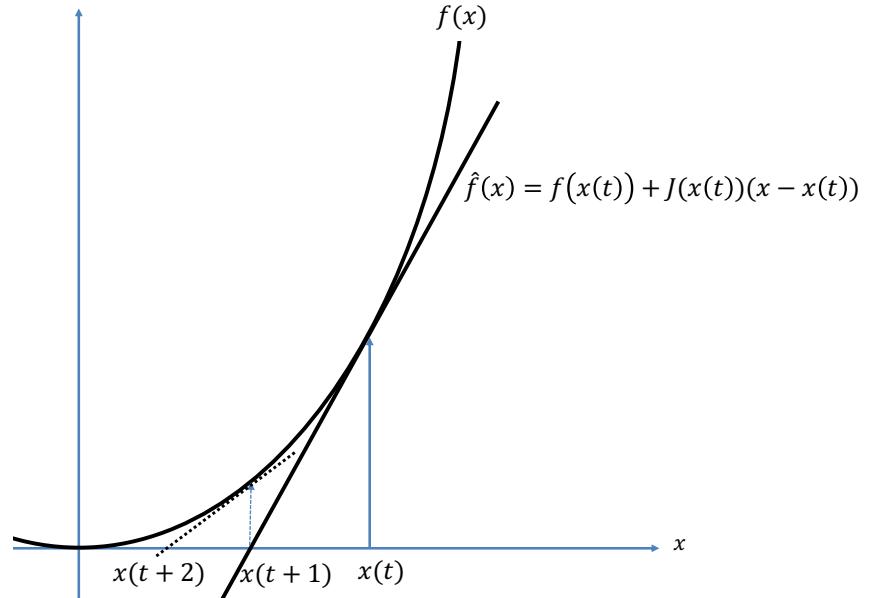
$$x(t+1) := x(t) - (J(x(t)))^{-1} f(x(t))$$



Computational methods

Newton-Raphson algorithm

Kantorovic Theorem

Consider $f : D \rightarrow \mathbb{R}^n$ where $D \subseteq \mathbb{R}^n$ is an open convex set. Suppose

- f is differentiable and ∇f is Lipschitz on D , i.e., $\|\nabla f(y) - \nabla f(x)\| \leq L\|y - x\|$
- $x_0 \in D$ and $\nabla f(x_0)$ is invertible

Let $\beta \geq \left\| (\nabla f(x_0))^{-1} \right\|$, $\eta \geq \left\| (\nabla f(x_0))^{-1} f(x_0) \right\|$ and

$$h := \beta\eta L, \quad r := \frac{1 - \sqrt{1 - 2h}}{h} \eta$$

Computational methods

Newton-Raphson algorithm

Kantorovic Theorem

Consider $f : D \rightarrow \mathbb{R}^n$ where $D \subseteq \mathbb{R}^n$ is an open convex set. Suppose

- f is differentiable and ∇f is Lipschitz on D , i.e., $\|\nabla f(y) - \nabla f(x)\| \leq L\|y - x\|$
- $x_0 \in D$ and $\nabla f(x_0)$ is invertible

If the closed ball $B_r(x_0) \subseteq D$ and $h \leq 1/2$, then Newton iteration

$$x(t+1) := x(t) - (\nabla f(x(t)))^{-1} f(x(t))$$

converges to a solution $x^* \in B_r(x_0)$ of $f(x) = 0$

Newton-Raphson converges if it starts close to a solution, often quadratically

Computational methods

Newton-Raphson algorithm

Apply to power flow equations in polar form:

$$p_j(\theta, |V|) = p_j, \quad j \in N$$

$$q_j(\theta, |V|) = q_j, \quad j \in N_{pq}$$

where

$$p_j(\theta, |V|) := \left(\sum_{k=0}^N g_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| \left(g_{jk} \cos \theta_{jk} + b_{jk} \sin \theta_{jk} \right)$$

$$q_j(\theta, |V|) := - \left(\sum_{k=0}^N b_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| \left(g_{jk} \sin \theta_{jk} - b_{jk} \cos \theta_{jk} \right)$$

Computational methods

Newton-Raphson algorithm

Define $f: \mathbb{R}^{N+N_{qp}} \rightarrow \mathbb{R}^{N+N_{qp}}$

$$f(\theta, |V|) := \begin{bmatrix} \Delta p(\theta, |V|) \\ \Delta q(\theta, |V|) \end{bmatrix} := \begin{bmatrix} p(\theta, |V|) - p \\ q(\theta, |V|) - q \end{bmatrix}$$

with

$$J(\theta, |V|) := \begin{bmatrix} \frac{\partial p}{\partial \theta} & \frac{\partial p}{\partial |V|} \\ \frac{\partial q}{\partial \theta} & \frac{\partial q}{\partial |V|} \end{bmatrix}$$

Computational methods

Newton-Raphson algorithm

1. Initialization: choose $(\theta(0), |V(0)|)$
2. Iterate until stopping criteria

(a) Determine $(\Delta\theta(t), \Delta|V|(t))$ from

$$J(\theta(t), |V|(t)) \begin{bmatrix} \Delta\theta(t) \\ \Delta|V|(t) \end{bmatrix} = - \begin{bmatrix} \Delta p(\theta(t), |V|(t)) \\ \Delta q(\theta(t), |V|(t)) \end{bmatrix}$$

(b) Set

$$\begin{bmatrix} \theta(t+1) \\ |V|(t+1) \end{bmatrix} := \begin{bmatrix} \theta(t) \\ |V|(t) \end{bmatrix} + \begin{bmatrix} \Delta\theta(t) \\ \Delta|V|(t) \end{bmatrix}$$

Computational methods

Fast Decoupled algorithm

Key observation: the Jacobian is roughly block-diagonal

$$J(\theta, |V|) := \begin{bmatrix} \frac{\partial p}{\partial \theta} & \frac{\partial p}{\partial |V|} \\ \frac{\partial q}{\partial \theta} & \frac{\partial q}{\partial |V|} \end{bmatrix} \approx \begin{bmatrix} \frac{\partial p}{\partial \theta} & 0 \\ 0 & \frac{\partial q}{\partial |V|} \end{bmatrix}$$

i.e., decoupling between p and $|V|$, and between q and θ

Computational methods

Fast Decoupled algorithm

Key observation: the Jacobian is roughly block-diagonal

$$J(\theta, |V|) := \begin{bmatrix} \frac{\partial p}{\partial \theta} & \frac{\partial p}{\partial |V|} \\ \frac{\partial q}{\partial \theta} & \frac{\partial q}{\partial |V|} \end{bmatrix} \approx \begin{bmatrix} \frac{\partial p}{\partial \theta} & 0 \\ 0 & \frac{\partial q}{\partial |V|} \end{bmatrix}$$

i.e., decoupling between p and $|V|$, and between q and θ

This simplifies the computation of $\Delta x(t)$

$$\frac{\partial p}{\partial \theta}(\theta(t), |V|(t)) \Delta \theta(t) = -\Delta p(\theta(t), |V|(t))$$

$$\frac{\partial q}{\partial |V|}(\theta(t), |V|(t)) \Delta |V|(t) = -\Delta q(\theta(t), |V|(t))$$

Computational methods

Fast Decoupled algorithm

Decoupling assumption: $g_{jk} = 0, \sin \theta_{jk} = 0$

$$\frac{\partial p_j}{\partial |V_k|} = \begin{cases} -|V_j| \left(g_{jk} \cos \theta_{jk} + b_{jk} \sin \theta_{jk} \right), & j \neq k \\ \frac{p_j(\theta, |V|)}{|V_j|} + \left(\sum_i g_{ji} \right) |V_j|, & j = k \end{cases}$$

$$g_{jk} = 0, \sin \theta_{jk} = 0, p_j(\theta, |V|) = 0 \Rightarrow \frac{\partial p}{\partial |V|} = 0$$

Computational methods

Fast Decoupled algorithm

Decoupling assumption: $g_{jk} = 0, \sin \theta_{jk} = 0$

$$\frac{\partial q_j}{\partial \theta_k} = \begin{cases} |V_j| |V_k| \left(g_{jk} \cos \theta_{jk} + b_{jk} \sin \theta_{jk} \right), & j \neq k \\ p_j(\theta, |V|) - \left(\sum_i g_{ji} \right) |V_j|^2, & j = k \end{cases}$$

$$g_{jk} = 0, \sin \theta_{jk} = 0, p_j(\theta, |V|) = 0 \Rightarrow \frac{\partial q}{\partial \theta} = 0$$

Summary

1. Component models
 - Single-phase devices, line, transformer
2. Network models
 - VI relation (admittance matrix Y), Vs relation (power flow models)
3. Computation methods
 - Gauss-Seidel algorithm, Newton-Raphson algorithm, Fast decoupled algorithm